


## Active Microwave Circuits

# Noise Analysis in Microwave Circuits

## Part II

© copyright 1997-2006 R. W. Jackson
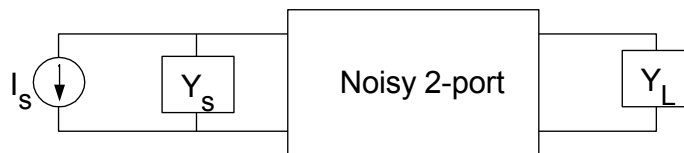
### Dependence of Noise Figure on Source Admittance




Will show  $F = F_{\min} + (R_n / G_s) |Y_s - Y_{\text{opt}}|^2$   
for any linear 2-port


$F_{\min}$ ,  $R_n$ ,  $G_{\text{opt}}$ ,  $B_{\text{opt}}$  are the noise parameters
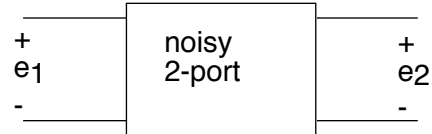
### Thevenin-Norton Representations of Noisy 2-Ports

$e_1, e_2$  are open circuit noise voltages




Thevenin equivalent

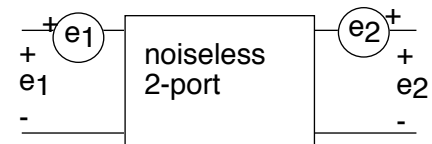

Thevenin-Norton equiv.


$$e_2 = -i Z_{21}$$

$$e_1 = -i Z_{11} + e$$

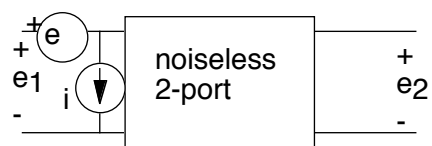

Solve for  $i, e$  in terms of  $e_1, e_2$
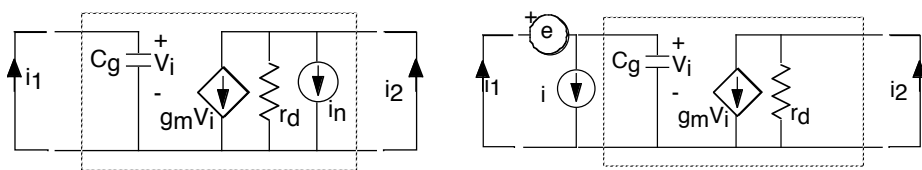
### Equivalent Noise Sources - an example



$$i_2 = i_n \quad \xrightarrow{\text{equate and solve for } e} \quad i_2 = g_m V_i = -g_m e$$


$$i_1 = 0 \quad \xrightarrow{\text{equate and solve for } i} \quad i_1 = i - j\omega C_g e$$

$$\underline{e = \frac{-i_n}{g_m}} \quad \underline{i = j\omega C_g e = \frac{-j\omega C_g}{g_m} i_n}$$

Equivalent noise sources  
in terms of model noise  
sources
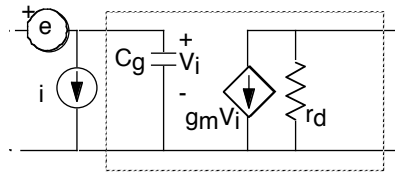
### Example- continued

$$e = \frac{-i_n}{g_m} \quad i = j\omega C_g e = \frac{-j\omega C_g}{g_m} i_n$$



Write in terms of noise notation


$$\overline{|e|^2} = \frac{\overline{|i_n|^2}}{g_m^2} \quad \overline{|i|^2} = \left( \frac{\omega C_g}{g_m} \right)^2 \overline{|i_n|^2} \quad \overline{ei^*} = \left( -j\omega C_g / g_m \right) \overline{|i_n|^2}$$

Derive for yourself the correlation coefficient, C.

Note e and i are uncorrelated since they are 90° out of phase.

This results in C being imaginary and  $\text{Re}(C) = 0$  (see lecture 9)

### Thevenin-Norton Equivalent

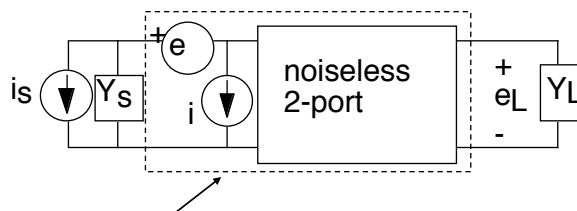


Thevenin-Norton equivalent of a noisy 2-port


- e and i are functions of impedances and noise sources internal to the 2-port

- e and i are specified by  $\overline{|e|^2}, \overline{|i|^2}, \overline{ei^*}$

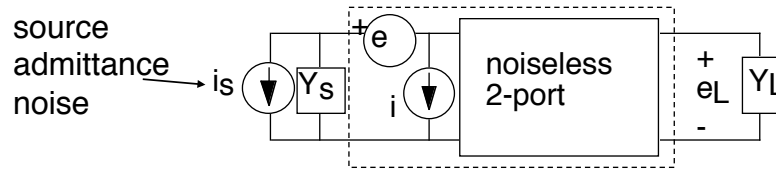
### Calculation of Noise Temp. in terms of $e$ and $i$



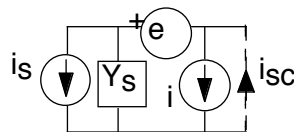First create Norton equivalent of everything on the input




all sources

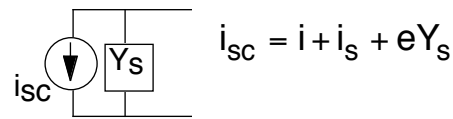

Norton equivalent
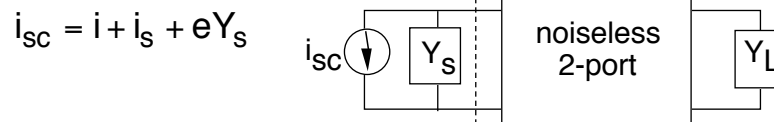
### Noise temperature i/t/o sources $i$ , $e$



Source appears "hotter" because of  $e$  &  $i$

$$P_{av} = \frac{\overline{|i_{sc}|^2}}{4 \operatorname{Re}(Y_s)} = \frac{\overline{|i + i_s + eY_s|^2}}{4 \operatorname{Re}(Y_s)} = k(T_0 + T_n)\Delta f$$

$$\text{noise temp.} = \frac{P_{av}|_{i_s=0}}{k\Delta f} = T_n = \frac{\overline{|i + eY_s|^2}}{4k\Delta f \operatorname{Re}(Y_s)}$$


### Noise Factor i/t/o e and i

It's easy to go from noise temp to noise factor

$$F = 1 + \frac{T_n}{T_o} = 1 + \frac{|i + eY_s|^2}{4kT_o\Delta f \text{Re}(Y_s)}$$

- Shows how F varies versus  $Y_s$  for any linear 2-port
- Need  $\overline{|e|^2}, \overline{|i|^2}, \overline{ei^*}$  to specify the equation (4 numbers)
- Form is not convenient as it stands

### A More Convenient Form

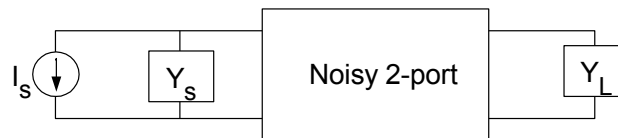

Will show  $F = F_{\min} + (R_n / G_s) |Y_s - Y_{\text{opt}}|^2$

$F_{\min}, R_n, G_{\text{opt}}, B_{\text{opt}}$  are the noise parameters

These four numbers are derived from the four numbers,  
 $\overline{|e|^2}, \overline{|i|^2}, \overline{ei^*}$

### Derivation of Noise Equation

$$F = 1 + \frac{(\bar{i} + eY_s)(\bar{i}^* + e^*Y_s^*)}{4kT_o\Delta f \text{Re}(Y_s)}$$

$$= 1 + \frac{|\bar{i}|^2 + \bar{e}\bar{i}^*Y_s + \bar{e}^*\bar{i}Y_s^* + |e|^2|Y_s|^2}{4kT_o\Delta f \text{Re}(Y_s)}$$

Remember correl coef.

$$C = C_r + jC_i \equiv \frac{e\bar{i}^*}{\sqrt{|e|^2|\bar{i}|^2}}$$

Normalize admittance

$$\tilde{Y}_s = \tilde{G}_s + j\tilde{B}_s \equiv Y_s \sqrt{\frac{|e|^2}{|\bar{i}|^2}}$$

$$F = 1 + \frac{\sqrt{|e|^2|\bar{i}|^2}}{4kT_o\Delta f} \frac{\tilde{G}_s^2 + \tilde{B}_s^2 + 2C_r\tilde{G}_s - 2C_i\tilde{B}_s + 1}{\tilde{G}_s}$$

### Choosing Admittance to Minimize F

$$F = 1 + \frac{\sqrt{|e|^2|\bar{i}|^2}}{4kT_o\Delta f} \frac{\tilde{G}_s^2 + \tilde{B}_s^2 + 2C_r\tilde{G}_s - 2C_i\tilde{B}_s + 1}{\tilde{G}_s}$$

Find minimum versus  $B_s$  in usual manner ( $dF/dB_s = 0$ )

$$\tilde{B}_{s,\min} = C_i \equiv \tilde{B}_{\text{opt}}$$

Find minimum versus  $G_s$

$$\tilde{G}_{s,\min} = \sqrt{1 - C_i^2} \equiv \tilde{G}_{\text{opt}}$$

Insert back in equation to get minimum F

$$F_{\min} \equiv 1 + \frac{\sqrt{|e|^2|\bar{i}|^2}}{2kT_o\Delta f} \left( \sqrt{1 - C_i^2} + C_r \right)$$

Rewrite Expression for F i/t/o minimum parameters

$$F - F_{\min} = \frac{\sqrt{|e|^2 |i|^2}}{4kT_0 \Delta f} \frac{\tilde{G}_S^2 - \tilde{G}_S 2\sqrt{1-C_i^2} + \tilde{B}_S^2 - 2C_i \tilde{B}_S + 1}{\tilde{G}_S}$$

$$= \frac{\sqrt{|e|^2 |i|^2}}{4k\Delta f} \frac{(\tilde{G}_S - \tilde{G}_{\text{opt}})^2 + (\tilde{B}_S - \tilde{B}_{\text{opt}})^2}{\tilde{G}_S}$$

un-normalize

$$\tilde{Y}_S \equiv Y_S \sqrt{\frac{|e|^2}{|i|^2}} \quad \tilde{Y}_{\text{opt}} \equiv Y_{\text{opt}} \sqrt{\frac{|e|^2}{|i|^2}}$$

$$F - F_{\min} = \frac{|e|^2}{4kT_0 \Delta f} \frac{(G_S - G_{\text{opt}})^2 + (B_S - B_{\text{opt}})^2}{B_S}$$

Final Form

$$F - F_{\min} = R_n \frac{(G_S - G_{\text{opt}})^2 + (B_S - B_{\text{opt}})^2}{B_S}$$

Noise parameters


$$F_{\min} \equiv 1 + \frac{\sqrt{|e|^2 |i|^2}}{2kT_0 \Delta f} (\sqrt{1-C_i^2} + C_r)$$

$$R_n \equiv \frac{|e|^2}{4kT_0 \Delta f}$$

$$G_{\text{opt}} \equiv \sqrt{\frac{|i|^2}{|e|^2}} \sqrt{1-C_i^2} \quad B_{\text{opt}} \equiv \sqrt{\frac{|i|^2}{|e|^2}} C_i$$

$$C_r + jC_i \equiv \frac{\overline{ei}^*}{\sqrt{|e|^2 |i|^2}}$$
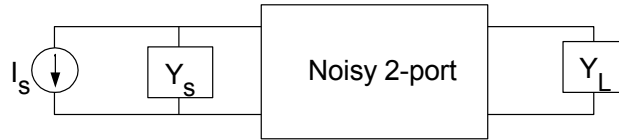
### General Form Noise Figure of Two Port




$$F = F_{\min} + R_n \frac{|Y_s - Y_{\text{opt}}|^2}{G_s}$$

$F_{\min}$ ,  $R_n$ ,  $G_{\text{opt}}$ ,  $B_{\text{opt}}$  are the noise parameters

### Example: an OP-AMP

The noise spec. for op-amps often includes  $\overline{|e|^2}, \overline{|i|^2}$ . These sources are uncorrelated at low, non microwave, frequencies.

For example at 10KHz a 741 opamp has

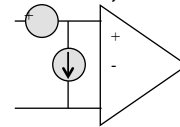

$$\overline{|e|^2} / \Delta f = 5 \times 10^{-16} \text{ V}^2 / \text{Hz} \quad \overline{|i|^2} / \Delta f = 3 \times 10^{-25} \text{ A}^2 / \text{Hz}$$

Using these numbers we get


$$F_{\min} = 1 + \frac{\sqrt{\overline{|e|^2} \overline{|i|^2}}}{2kT_o \Delta f} \left( \sqrt{1 - C_i^2} + C_r \right) = 2.53$$

Of course this ignores the feedback normally used with op-amps


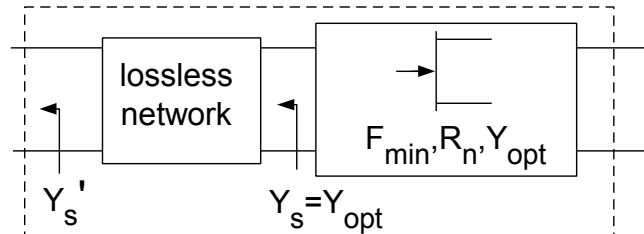
### Invariants

- Adding a lossless 2-port to a noisy 2-port will not change  $F_{\min}$ . (A  $Y_s'$  can always be found to make  $Y_s = Y_{\text{opt}}$ )



- Adding a lossless 2-port to a noisy 2-port will not change the product  $(R_n \times G_{\text{opt}})$ .

$$(R'_n \times G'_{\text{opt}}) = (R_n \times G_{\text{opt}}) = N$$

### Invariants

The minimum noise measure,  $M_{\min}$ , is invariant for any lossless embedding network (even including feedback)

(Haus & Adler, Proc. IEEE, Aug. 1958)

$$T_{\min} < 4NT_o \text{ (Pospieszalski, MTT Trans. Sept. 1989)}$$

### Noise Figure Expression in terms of $\Gamma$

$$Y_s = Y_o \frac{1 - \Gamma_s}{1 + \Gamma_s} \quad Y_{opt} = Y_o \frac{1 - \Gamma_{opt}}{1 + \Gamma_{opt}}$$

$$F = F_{min} + 4r_n \frac{|\Gamma_s - \Gamma_{opt}|^2}{|1 + \Gamma_{opt}|^2 (1 - |\Gamma_s|^2)} \quad , r_n \equiv \frac{R_n}{Z_o}$$


Find  $R_n$ ,  $F_{min}$ ,  $\Gamma_{opt}$  experimentally by measuring  $F$  for 4 or more known  $\Gamma_s$

Fit equation to measurements.

### Noise Parameter Measurement

Several  $Y_s$  presented to device.


Noise fig. measured at each

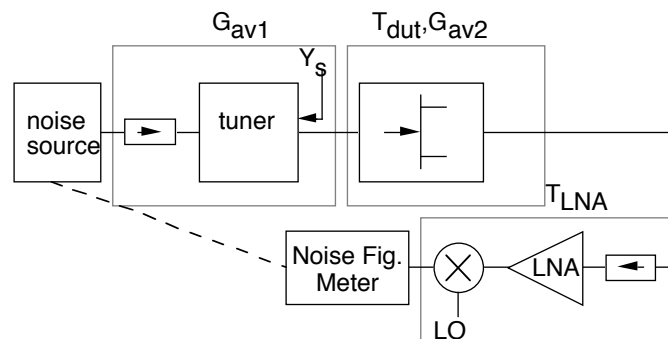

$$F_{meas} = \frac{1}{G_{av1}} + \frac{F_{dut} - 1}{G_{av1}} + \frac{F_{LNA} - 1}{G_{av1}G_{av2}}$$

need to de-embed  $F_{dut}$  from measurement

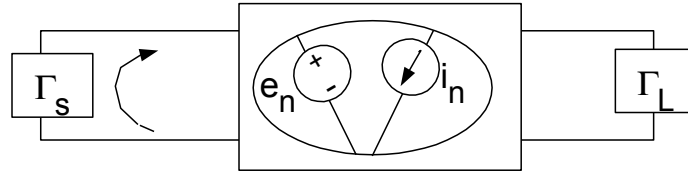
### Interpretation of Effect of Source on Noise



To minimize noise delivered to load,  $\Gamma_s$  is adjusted so as to reflect noise through 2-port and partially cancel noise emitted from port 2
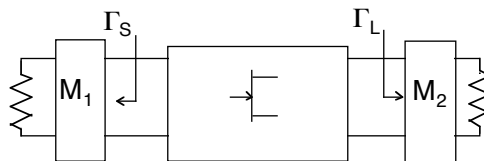
### Low Noise Amplifier Design

Previously  $\Gamma_s$ ,  $\Gamma_L$  chosen for gain and match




$$F = F_{\min} + 4r_n \frac{|\Gamma_s - \Gamma_{\text{opt}}|^2}{|1 + \Gamma_{\text{opt}}|^2 (1 - |\Gamma_s|^2)}, \quad r_n \equiv \frac{R_n}{Z_o}$$

## Amplifier vs. Device: Gain and Noise Figure

For lossless matching networks

$$F_{M1} = \frac{1}{G_{avM1}} = 1$$

$$F_{M2} = \frac{1}{G_{avM2}} = 1$$

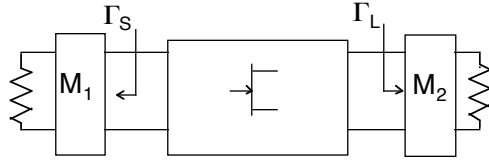

$$G_{avLNA} = G_{avM1} G_{avdev} G_{avM2} = G_{avdev}$$

$$F_{LNA} = F_{M1} + \frac{F_{dev} - 1}{G_{avM1}} + \frac{F_{M2} - 1}{G_{avM1} G_{avdev}} = F_{dev}$$

If  $M_1, M_2$  lossless,  
amplifier available  
gain and noise  
figure = device  
available gain and  
noise figure

## Noise Circles

Noise equation gives noise figure resulting from  $\Gamma_S$

$$F = F_{min} + 4r_n \frac{|\Gamma_S - \Gamma_{opt}|^2}{|1 + \Gamma_{opt}|^2 (1 - |\Gamma_S|^2)}, \quad r_n \equiv \frac{R_n}{Z_o}$$

The reverse problem is: Find a set of  $\Gamma_S$  that give a specified noise figure.

A locus of  $\Gamma_S$  points that all give the same noise figure form a noise circle in the  $\Gamma_S$  plane.

### Noise Circles on the Smith Chart


center of  $i'$  th circle

$$C_{fi} = \frac{\Gamma_{opt}}{1 + N_i}$$

radius of  $i'$  th circle

$$r_{fi} = \frac{1}{1 + N_i} \sqrt{N_i(1 - |\Gamma_{opt}|^2) + N_i^2}$$


$$N_i \equiv \frac{(F_i - F_{min})|1 + \Gamma_{opt}|^2}{4r_n}$$

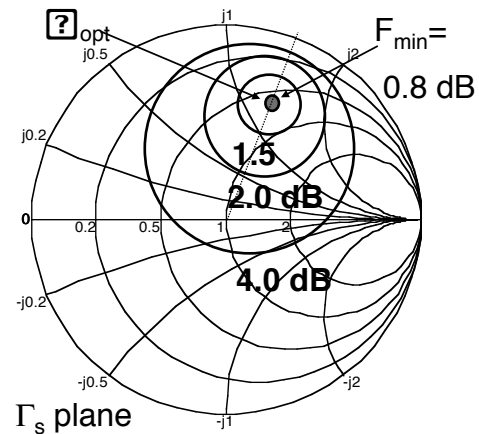

Derivation is similar to previous derivations that use circles in the Smith Chart
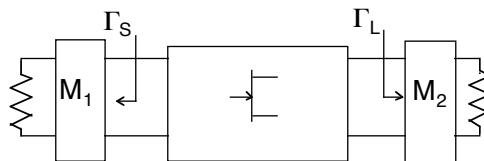
### Low Noise Amplifier Design

Previously  $\Gamma_S, \Gamma_L$   
chosen for gain  
and match



Different choice for minimum noise

$$\Gamma_S = \Gamma_{opt} \quad (\text{minimum noise})$$


$$\Gamma_L = \left( S_{22} + \frac{S_{21}S_{12}\Gamma_S}{1 - S_{11}\Gamma_S} \right)^* \quad (\text{good output match})$$

input match sacrificed

## Gain Versus Noise Trade

- ✧ Choosing  $\Gamma_s = \Gamma_{opt}$  trades (i) gain and (ii) input match for good noise performance
- ✧ The associated gain of a device is the gain achieved when  $\Gamma_s = \Gamma_{opt}$  and  $\Gamma_L = \Gamma_{out}^*$
- ✧ Often a designer will trade a little noise performance for improved gain
- ✧ To evaluate gain-noise trades plot noise and available gain circles on Smith charts
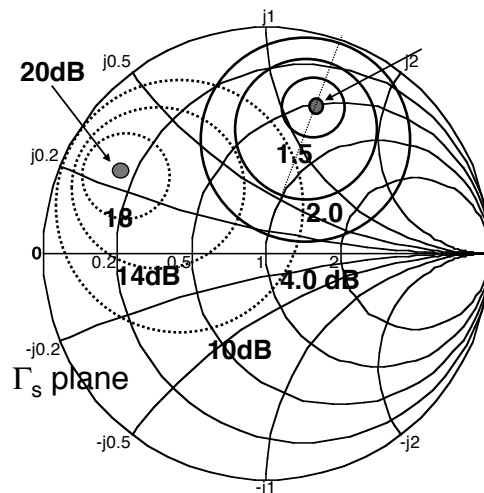
## Noise and Available Gain Circles in $\Gamma_s$ Plane



Note *associated gain*

✧ Choosing  $\Gamma_s = \Gamma_{opt}$  gives  $F = F_{min} = .8$  dB and  $G_T = G_{assoc} < 10$  dB

✧ Choosing  $\Gamma_s = \Gamma_{sm}$  gives  $F > 4$  dB and  $G_T = G_{mag} = 20$  dB


✧ Choosing  $\Gamma_s = 0.5 \angle 100^\circ$  gives  $F = 2$  dB and  $G_T = 14$  dB

### Equations for Available Gain circles

$$C_A = \frac{g_a(S_{11} - \Delta S_{22}^*)^*}{1 + g_a(|S_{11}|^2 - |\Delta|^2)}, \quad g_a = \frac{G_{AV}}{|S_{21}|^2}, \quad r_A = \frac{\left[1 - 2K|S_{21}S_{21}|g_a + |S_{21}S_{21}|^2 g_a^2\right]^{\frac{1}{2}}}{|1 + g_a(|S_{11}|^2 - |\Delta|^2)|}$$
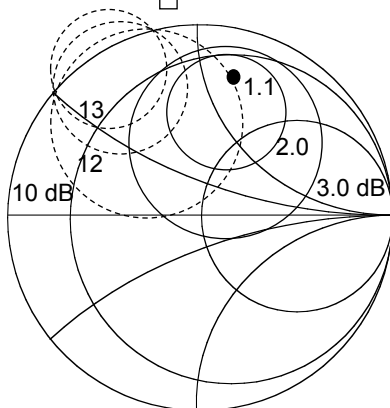
### LNA with Potentially Unstable Device


- ✱ Design to achieve at least 12 dB gain and < 2.5 dB noise figure



- ✱ Choosing  $\Gamma_S = .45 \angle 110^\circ$  gives  $F = 2$  dB,  $G_T = 12$  dB

- ✱ Choosing  $\Gamma_L = 0.56 \angle 66^\circ$  matches output  $\Gamma_L = \Gamma_{out}^*$

- ✱ A possible realization

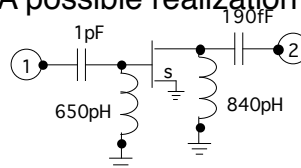

- ✱ S parameters of over-all amplifier:  
 $|S_{21}| = 12.1$  dB  
 $|S_{11}| = -1.0$  dB  $|S_{22}| = -42$  dB  
 $F = 1.84$  dB

### Notes on LNA example


@ 10 GHz

$$\begin{aligned} S_{11} &= 0.806 \angle -96^\circ & S_{21} &= 2.24 \angle 99^\circ \\ S_{12} &= 0.115 \angle 38^\circ & S_{22} &= 0.553 \angle -43^\circ \end{aligned}$$

$$\begin{aligned} F_{\min} &= 1.12 \text{ dB} \\ \Gamma_{\text{opt}} &= 0.71 \angle 74.0^\circ \\ r_n &= 0.458 \end{aligned}$$
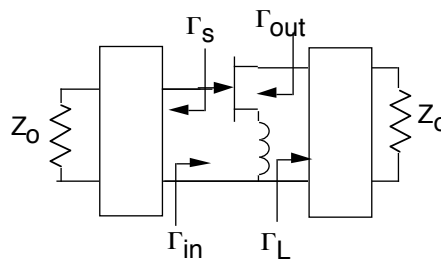
### Use of Source Inductance in LNA design

Find source inductance and  $\Gamma_L$  such that  $\Gamma_{\text{in}} = \Gamma_{\text{opt}}^*$  with good gain



- Source inductance reduces  $F_{\min}$ , but not much
- Source inductance reduces  $G_{\text{mag}}$  (or  $G_{\text{msg}}$ )
- Goal is to get a good input match **and** a good noise figure



### Procedure

- ✿ Pick a trial inductance
- ✿ Compute a new  $\Gamma_{\text{opt}}$
- ✿ Is there a  $\Gamma_L$  that gives  $\Gamma_{\text{in}} = \Gamma_{\text{opt}}^* = S_{11} + \frac{S_{12}S_{21}\Gamma_L}{1 - S_{22}\Gamma_L}$
- ✿ For this  $\Gamma_L$  compute gain - enough?
- ✿ Stability
- ✿ If not good, increase inductance and try again

### Example

	S and noise parameters of FET at 10 GHz	After adding 0.2 nH series L
S <sub>11</sub>	0.76<-87°	0.53<-76°
S <sub>21</sub>	2.2<94°	2.08<94°
S <sub>12</sub>	0.11<52°	0.13<52°
S <sub>22</sub>	0.54<-50°	0.57<-28°
F <sub>min</sub>	1.5 dB	1.47 dB ←
$\Gamma_{\text{opt}}$	0.50<81°	0.40<92°
R <sub>n</sub>	0.37(50)	0.26(50) ←
G <sub>msg</sub>	13 dB	12 dB ←

Note: gain went down, noise circles spread, F<sub>min</sub> stays same

Find  $\Gamma_L$  and check gain

$$\Gamma_{in} = S_{11} + \frac{S_{21}S_{12}\Gamma_L}{1 - S_{22}\Gamma_L} = \Gamma_{opt}^*$$

Solve for  $\Gamma_L$

$$\Gamma_L = \frac{\Gamma_{in} - S_{11}}{-\Delta + S_{22}\Gamma_{in}} \bigg|_{\Gamma_{in} = \Gamma_{opt}^*} = .40 \angle -92^\circ$$


$$\Gamma_L = .58 \angle -22.7$$

Evaluate gain

$$G_p = \frac{1}{1 - |\Gamma_{in}|^2} |S_{21}|^2 \frac{1 - |\Gamma_L|^2}{|1 - S_{22}\Gamma_L|^2}$$

$$= \underline{\underline{7\text{db}}}$$

### Final Results

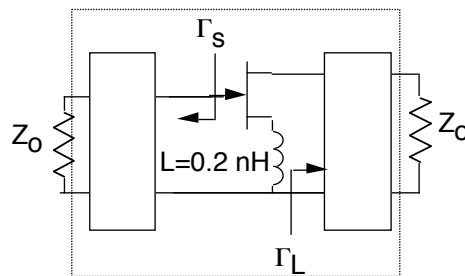

$$\Gamma_s = .40 \angle 92^\circ$$

$$\Gamma_L = .58 \angle -22.7$$

•poor match at output

•good match at input

•good noise figure

•mediocre gain

$$|S_{11}| = .004$$

$$|S_{12}| = .134$$

$$|S_{21}| = 2.22 \text{ (6.9 dB)}$$


$$|S_{22}| = .71$$

$$F_{min} = 1.5 \text{ dB}$$

$$\Gamma_s = .40 \angle 92^\circ$$
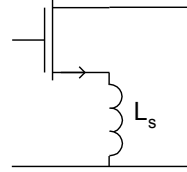
## Inductive Source Degeneration in CMOS LNA


Adding inductance simplifies matching without reducing F



Input impedance

$$v_T = i_G \frac{1}{sC_{gs}} + sL_s(i_G + g_m V) \quad V = \frac{i_G}{sC_{gs}}$$

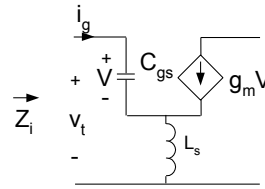
$$Z_{in} = \frac{v_T}{i_G} = \frac{1}{j\omega C_{gs}} + j\omega L_s + \frac{g_m L_s}{C_{gs}}$$



$L_s$  set to make  $\text{Re}(Z_i)$  equal source resistance,  $R_s$
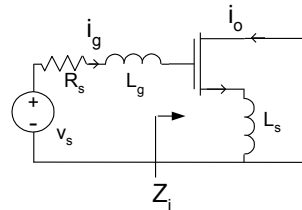
## $L_g$ Added

$L_g$  is added to resonate  $\text{Im}(Z_i)$



$$i_G = \frac{V_s}{R_s + j\omega L_g + Z_i} = \frac{V_s}{R_s + \frac{g_m L_s}{C_{gs}} + j \left( \omega L_s + \omega L_g - \frac{1}{\omega C_{gs}} \right)}$$

$$i_o = g_m V = g_m \frac{i_G}{j\omega C_{gs}} = \frac{g_m}{j\omega C_{gs}} \frac{V_s}{R_s + \frac{g_m L_s}{C_{gs}}}$$

$$i_o = \frac{g_m V_s}{j\omega C_{gs} 2R_s}$$

$$|i_o| = Q_{in} g_m V_s$$

The  $g_m$  of the circuit is enhanced by the input circuit Q

## CMOS Noise Model

$$\overline{|i_{nd}|^2} = 4\kappa T \gamma g_{do} \Delta f$$

$$\overline{|v_{ng}|^2} = 4\kappa T \delta r_g \Delta f$$

$$C = \frac{\overline{v_{ng} i_{nd}^*}}{\sqrt{\overline{|v_{ng}|^2} \overline{|i_{nd}|^2}}}$$


For long channel CMOS

$$\delta \approx 4/3 \quad \gamma \approx 2/3 \quad C \approx -j(.39)$$


$$r_g \approx 1/5 g_{do}$$

$g_{do}$  is drain source conductance at  $V_{ds} = V_{gs} - V_T$

$$g_{do} \approx g_m$$

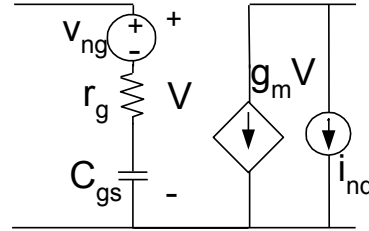
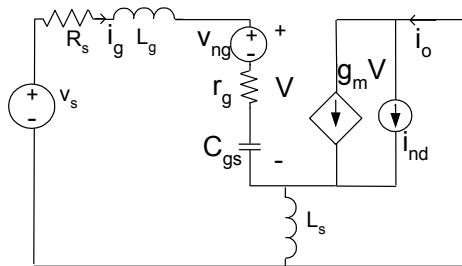
## Noise Figure Inductor Degenerated CMOS



To simplify algebra

$$V \approx \frac{i_g}{j\omega C_{gs}}$$

$$C \approx 0$$

$$\delta \approx 1$$

$$F = 1 + \frac{|i_o|_{v_s=0}^2}{|i_o|_{v_{ng}, i_{nd}=0}^2} = 1 + \frac{r_g}{R_s} + \frac{\omega^2}{\omega_T^2} R_s \gamma g_{do}$$

$$\omega_T \equiv \frac{g_m}{C_{gs}}$$

$$= 1 + \frac{1}{R_s 5 g_{do}} + \frac{\omega^2}{\omega_T^2} R_s \gamma g_{do}$$


$$r_g \approx 1/5 g_{do}$$

Derivation in HW solutions
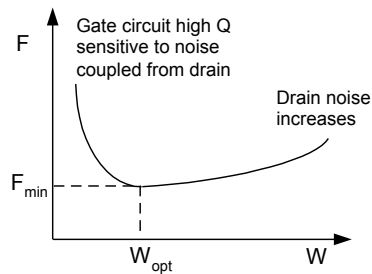
### Choosing width of device for $F_{\min}$

$$F = 1 + \frac{1}{R_s 5 g_{do}} + \frac{\omega^2}{\omega_T^2} R_s \gamma g_{do} \quad \omega_T \equiv \frac{g_m}{C_{gs}}$$

For a long channel device  $g_m = \frac{\partial i_d}{\partial v_{gs}} = \mu_n C_{ox} \frac{W}{L} (V_{GS} - V_T) \approx g_{do}$



$$(g_{do})_{\min} = \frac{\omega_T}{\omega} \frac{1}{R_s \sqrt{5\gamma}}$$

$$F_{\min} = 1 + \frac{\omega}{\omega_T} 2 \sqrt{\frac{\gamma}{5}}$$

### Example: $\omega/\omega_T = 0.25$ , $R_s = 50$ , $\gamma = 2$

$$(g_{do})_{\min} = \frac{\omega_T}{\omega} \frac{1}{R_s \sqrt{5\gamma}} = .025 \text{ S} \quad F_{\min} = 1 + \frac{\omega}{\omega_T} 2 \sqrt{\frac{\gamma}{5}} \rightarrow 1.1 \text{ dB}$$

For a long channel device

$$g_{do} = \mu_n C_{ox} \frac{W}{L} (V_{GS} - V_T)$$

$\swarrow \quad \nwarrow \quad \nwarrow \quad \swarrow$   
 $.04 \text{ m}^2/\text{V-s} \quad .015 \text{ F/m}^2 \quad .18 \text{ uM} \quad V_{OD} = .25 \text{ V}$

$$W_{\text{opt}} = 30 \text{ uM}$$

$$I_D = \frac{\mu_n C_{ox}}{2} \frac{W_{\text{opt}}}{L} V_{od}^2 = 6 \text{ mA}$$

## Noise Models for Devices

Used to determine noise parameters for:


- different frequency
- different size devices

Used to diagnose device noise behavior

Noise sources not frequency dependent

Noise sources depend on channel doping, device structure

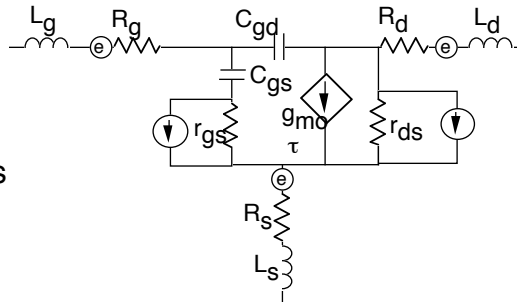
Can be found by fitting to measurements or theoretically


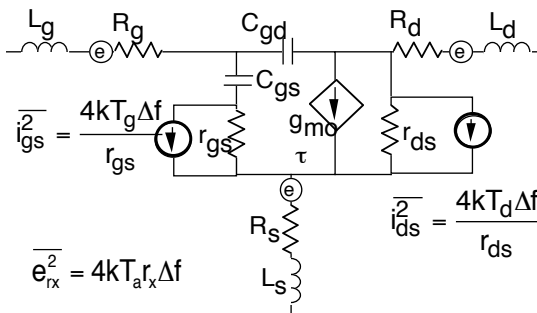
## FET Noise Model (Pospieszalski model)

$r_{ds}$  and  $r_{gs}$  at temperatures,  $T_d$  and  $T_g$


$T_d$  and  $T_g$  set by noise measurements at one frequency



$T_g$  usually near ambient,  $T_d$  is much higher (500-2000°K)

Other resistors have a thermal noise source in series having a value  $e_{rx}^2 = 4kT_a r_x \Delta f$  ( $T_a$  is ambient temp. )

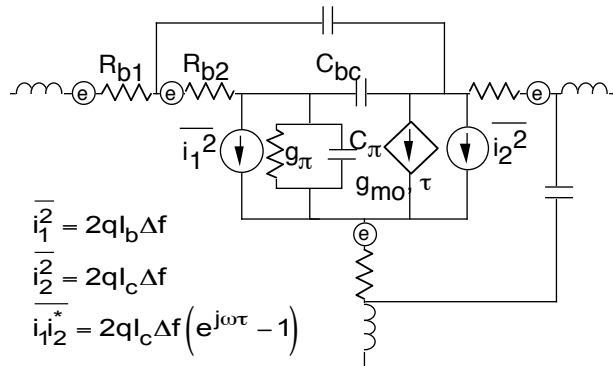Model determined from physical characteristics - no fitting once circuit model is determined



Each resistor has a thermal noise source in series with it having a value  $|e_R|^2 = 4kTR\Delta f$

University of Massachusetts at Amherst - Active Microwave Circuits - Noise Analysis 45


- ✿ Transforming noise parameters
- ✿ Source inductance in LNA design
- ✿ Noise models for FET, HBT

Computationally Efficient Electronic-Circuit Noise Calculations," R. Rohrer, L. Nagel, R. Meyer, and L. Weber, IEEE Journal of Solid State Circuits, August 1971

## Supplemental Material
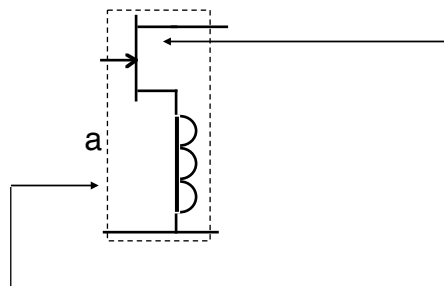
### Transforming Noise Parameters

Given the device parameters  $F_{\min}$ ,  $R_n$ ,  $G_{\text{opt}}$ ,  $B_{\text{opt}}$




Find the parameters  $F_{\min}^a$ ,  $R_n^a$ ,  $G_{\text{opt}}^a$ ,  $B_{\text{opt}}^a$

To find the noise parameters for the “a” circuit from the device parameters use thevenin, norton sources



### Reminder

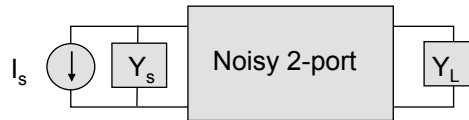


$$F = F_{\min} + (R_n / G_s) |Y_s - Y_{\text{opt}}|^2$$

The noise parameters,  $F_{\min}$ ,  $R_n$ ,  $G_{\text{opt}}$ ,  $B_{\text{opt}}$  can be derived from the four numbers,

$$\overline{|e|^2}, \overline{|i|^2}, \overline{ei^*}$$
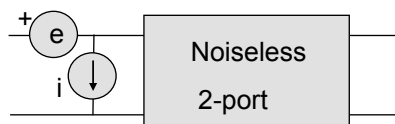
### Noise sources needed for combining noisy circuits



First go from noise parameters to equivalent sources

$$\begin{Bmatrix} F_{\min} \\ R_n \\ Y_{\text{opt}} \end{Bmatrix} \Rightarrow \begin{Bmatrix} \overline{|e|^2} \\ \overline{|i|^2} \\ C \end{Bmatrix} \quad \text{where} \quad C = C_r + jC_i \equiv \frac{\overline{ei^*}}{\sqrt{\overline{|e|^2}} \sqrt{\overline{|i|^2}}}$$

### Transformations

Sources  $\Rightarrow$  Noise Param.    Noise Param.  $\Rightarrow$  Sources

$$\begin{array}{l|l}
 R_n = \frac{\overline{|e|^2}}{4KT\Delta f} & \overline{|e|^2} = 4KT\Delta f R_n \\
 Y_{opt} = \frac{\sqrt{\overline{|i|^2}}}{\sqrt{\overline{|e|^2}}} \left[ \sqrt{1 - C_i^2} + jC_i \right] & \overline{|i|^2} = 4KT\Delta f R_n |Y_{opt}|^2 \\
 & C_i = \text{Im}[Y_{opt}] / |Y_{opt}| \\
 F_{min} = \frac{\sqrt{\overline{|i|^2} \overline{|e|^2}}}{2kT\Delta f} \left( \sqrt{1 - C_i^2} + C_r \right) + 1 & C_r = \frac{1}{|Y_{opt}|} \left[ \frac{F_{min} - 1}{2R_n} - \text{Re}(Y_{opt}) \right]
 \end{array}$$

### Where do transformations come from?

$$\begin{aligned}
 R_n = \frac{\overline{|e|^2}}{4KT\Delta f} & \Rightarrow \overline{|e|^2} = 4KT\Delta f R_n \\
 Y_{opt} = \frac{\sqrt{\overline{|i|^2}}}{\sqrt{\overline{|e|^2}}} \left[ \sqrt{1 - C_i^2} + jC_i \right] & \Rightarrow \overline{|i|^2} = |Y_{opt}|^2 \overline{|e|^2} \\
 & = 4KT\Delta f R_n |Y_{opt}|^2 \\
 \Rightarrow C_i = \sqrt{\frac{\overline{|e|^2}}{\overline{|i|^2}}} \text{Im}[Y_{opt}] & \\
 = \text{Im}[Y_{opt}] / |Y_{opt}| &
 \end{aligned}$$

### Algebra for Transformation (cont.)


$$F_{\min} = \frac{\sqrt{|i|^2 |e|^2}}{2kT\Delta f} \left( \sqrt{1 - C_i^2} + C_r \right) + 1 \Rightarrow C_r = (F_{\min} - 1) \frac{2kT\Delta f}{\sqrt{|i|^2 |e|^2}} - \sqrt{1 - C_i^2}$$

$$= \frac{F_{\min} - 1}{2R_n |Y_{\text{opt}}|} - \sqrt{1 - C_i^2}$$

$$C_r = \frac{1}{|Y_{\text{opt}}|} \left[ \frac{F_{\min} - 1}{2R_n} - \text{Re}(Y_{\text{opt}}) \right]$$


$$\sqrt{1 - C_i^2} = \sqrt{1 - \left( \frac{\text{Im}(Y_{\text{opt}})}{|Y_{\text{opt}}|} \right)^2} = \frac{1}{|Y_{\text{opt}}|} \sqrt{|Y_{\text{opt}}|^2 - \text{Im}(Y_{\text{opt}})^2} = \frac{\text{Re}(Y_{\text{opt}})}{|Y_{\text{opt}}|}$$
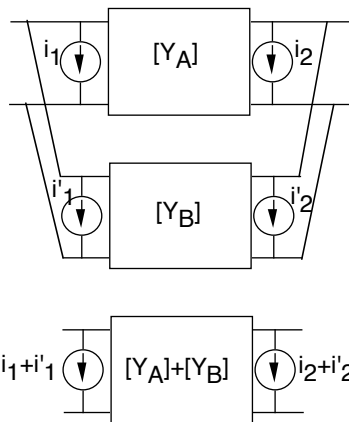
### Combined Noise Sources of Shunt Connected Circuit



Norton equivalent  
noise sources make  
shunt combinations  
easy
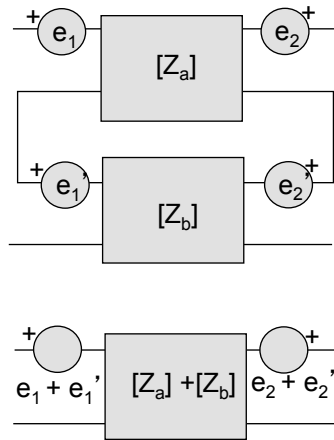
### Combined Noise Sources of Series Connected Circuit




Thevenin equivalents  
make series combinations  
easy

(Thevenin-Norton sources  
are appropriate for  
cascaded connections of  
noisy 2-ports)
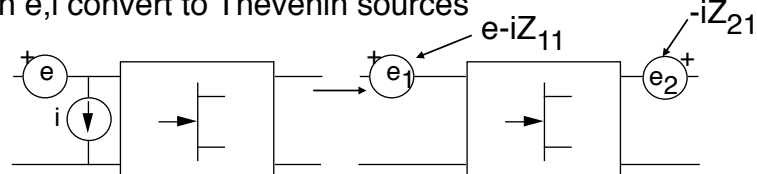
### Example: Effect of Series Feedback Inductance


- Given  $e, i$  convert to Thevenin sources




- sum Z matrix of FET to Z matrix of inductor

$$[Z^a] = [Z] + j\omega L \begin{bmatrix} 1 & 1 \\ 1 & 1 \end{bmatrix}$$

lossless inductor adds  
no noise

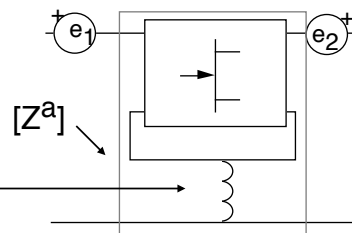

### Convert Back to Thevenin-Norton

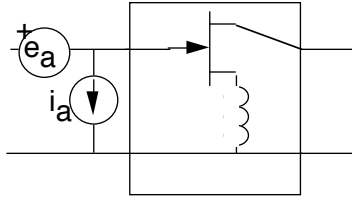

Solve for  $e_a, i_a$  i/t/o  $e_1, e_2$   
from last slide

Replace  $e_1, e_2$  with device  
noise sources  $e, i$

$$\begin{cases} e_a - i_a z_{11}^a = e_1 \\ -i_a z_{11}^a = e_2 \end{cases} \rightarrow \begin{cases} e_a = e_1 + \frac{-e_2}{z_{21}^a} z_{11}^a \\ i_a = \frac{-e_2}{z_{21}^a} \end{cases} \rightarrow \begin{cases} e_a = e - i z_{11} + \frac{i z_{21}}{z_{21}^a} z_{11} \\ i_a = \frac{i z_{21}}{z_{21}^a} \end{cases}$$

### Noise Transformation Matrix


$$e_a = e + \left[ -z_{11} + \frac{z_{11}^a}{z_{21}^a} \right] i$$

$$i_a = \frac{z_{21}}{z_{21}^a} i$$



$$\begin{bmatrix} e_a \\ i_a \end{bmatrix} = \begin{bmatrix} n_{11} & n_{12} \\ n_{21} & n_{22} \end{bmatrix} \begin{bmatrix} e \\ i \end{bmatrix}$$

noise transformation matrix

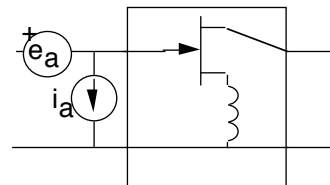

$$n_{11} = 1$$

$$n_{12} = -z_{11} + \frac{z_{11} + j\omega L}{z_{21} + j\omega L}$$

$$n_{21} = 0$$

$$n_{22} = \frac{z_{21}}{z_{21} + j\omega L}$$

### Noise Transformation Matrix

In this example, the circuit (inductor) added was lossless.

If the feedback circuit was lossy, the transformation matrix would look like,

$$\begin{bmatrix} e_a \\ i_a \end{bmatrix} = \begin{bmatrix} n_{11} & n_{12} \\ n_{21} & n_{22} \end{bmatrix} \begin{bmatrix} e \\ i \end{bmatrix} + \begin{bmatrix} n_{11}' & n_{12}' \\ n_{21}' & n_{22}' \end{bmatrix} \begin{bmatrix} e_n \\ i_n \end{bmatrix}$$

due to noise in feedback circuit

$$\overline{|e^a|^2} = \overline{|n_{11}e + n_{12}i|^2} \quad \text{Calculate Noise Amplitudes \& Correlation}$$

$$\begin{aligned} &= |n_{11}|^2 \overline{|e|^2} + n_{11}e(\overline{n_{12}i})^* + \overline{n_{12}i}(n_{11}e)^* + |n_{12}|^2 \overline{|i|^2} \\ &= |n_{11}|^2 \overline{|e|^2} + 2\text{Re}\left[n_{11}n_{12}^* C\sqrt{\overline{|e|^2}}\sqrt{\overline{|i|^2}}\right] + |n_{12}|^2 \overline{|i|^2} \end{aligned}$$

$$\overline{|i^a|^2} = \overline{|n_{21}e + n_{22}i|^2}$$

$$= |n_{21}|^2 \overline{|e|^2} + 2\text{Re}\left[n_{21}n_{22}^* C\sqrt{\overline{|e|^2}}\sqrt{\overline{|i|^2}}\right] + |n_{22}|^2 \overline{|i|^2}$$

$$\begin{aligned} C^a &= \frac{1}{\sqrt{\overline{|e^a|^2}}\sqrt{\overline{|i^a|^2}}} \overline{e^a i^a}^* = \frac{1}{\sqrt{\overline{|e^a|^2}}\sqrt{\overline{|i^a|^2}}} \overline{(n_{11}e + n_{12}i)(n_{21}e + n_{22}i)^*} \\ &\rightarrow = n_{11}n_{21}^* \overline{|e|^2} + n_{12}n_{21}^* \overline{ie}^* + n_{11}n_{22}^* \overline{ei}^* + n_{12}n_{22}^* \overline{|i|^2} \end{aligned}$$

### Finally, Calculate New Noise Parameters

$$Y_{\text{opt}}^a = \frac{\sqrt{|i^a|^2}}{\sqrt{|e^a|^2}} \left[ \sqrt{1 - (C_i^a)^2} + jC_i^a \right]$$

$$F_{\text{min}}^a = \frac{\sqrt{|i^a|^2} |e^a|^2}{2kT\Delta f} \left[ \sqrt{1 - (C_i^a)^2} + C_r^a \right] + 1$$

$$R_n^a = \frac{|e^a|^2}{4kT\Delta f}$$

### Summary

- ✿ Start with  $F_{\text{min}}$ ,  $R_n$ ,  $G_{\text{opt}}$ ,  $B_{\text{opt}}$  of FET
- ✿ Find  $|e|^2$ ,  $|i|^2$ ,  $C$  from formulas
- ✿ Find noise transformation matrix for circuit under study

$$\begin{Bmatrix} e \\ i \end{Bmatrix} \rightarrow \begin{Bmatrix} e^a \\ i^a \end{Bmatrix}$$

- ✿ Form  $|e^a|^2$ ,  $|i^a|^2$ ,  $C^a$
- ✿ Plug into formulas for  $F_{\text{min}}^a$ ,  $R_n^a$ ,  $G_{\text{opt}}^a$ ,  $B_{\text{opt}}^a$

(usually done by CAD)